



## ET 110/C13 – Electric Circuit Analysis

### Homework 6 – Parallel dc circuit (Due date: Monday - 10/24/16)

**YOU HAVE TO SHOW ALL WORK IN ORDER TO RECEIVE FULL CREDIT**


**Note: All answer must be in engineering notation rounded off to the hundredth**

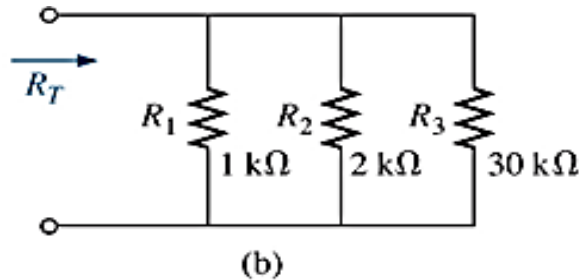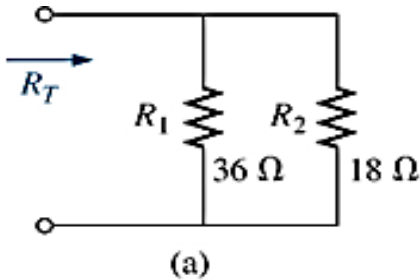1. Find the total resistance for each configuration parallel circuit (a = 5 pts, b = 6 pts)



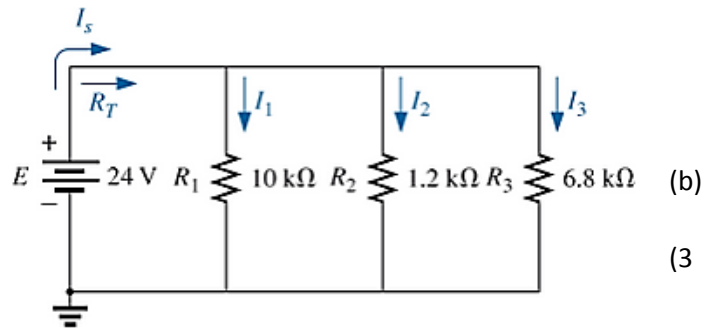
2. For the parallel circuit

- Find the current through each branch (6 pts)
- Find the total resistance (6 pts)
- Calculate current source  $I_s$  using the result of part (3) (3 pts)
- Find the source current using the result of part (a) (pts)




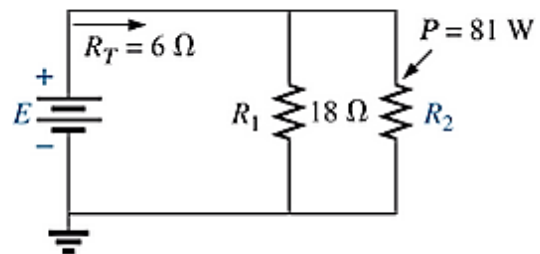3. Given the information provided

- The resistance  $R_2$  (5 pts)
- The supply voltage  $E$  (4 pts)




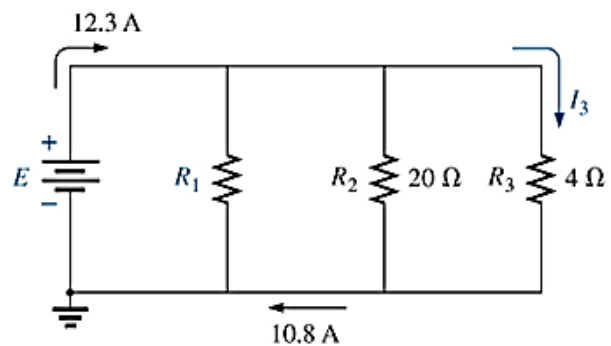4. Given the following parallel circuit, find the unknown quantities,  $E$ ,  $R_1$  and  $I_3$  (4 points each)




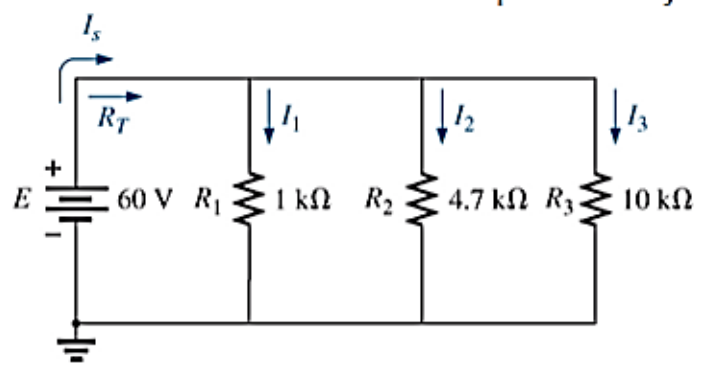5. For the following parallel circuit

- Find the total resistance and the current through each branch (6 pts)
- Find the power delivered to each resistor (6 pts)
- Calculate the power delivered by the source (3 pts)



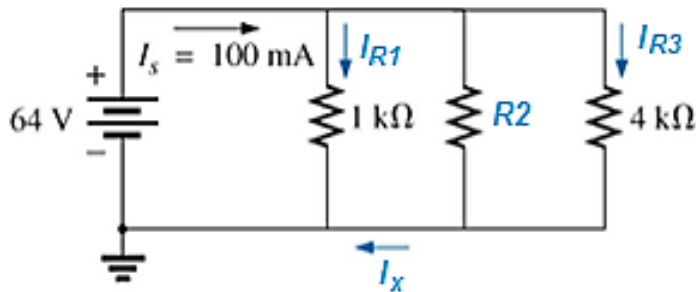6. Find the unknown quantities for the following parallel circuit,  $I_{R1}$ ,  $I_x$ ,  $I_{R3}$ ,  $R$  (4 points each)



7. Find the unknown quantities for the following parallel circuit,  $I_{R1}$ ,  $I_{R3}$ ,  $R_2$ ,  $R_3$ ,  $P_{R2}$ , and  $E$  (4 points each)

