

Queensborough Community College
The City University Of New York
Department of Engineering Technology

ET 110 – Introduction to circuit analysis

Pre-Exam2 Due date: Wednesday 10/26/16

Student's name: _____


Academic dishonesty is prohibited in The City University of New York and is punishable by penalties, including failing grades, suspension, and expulsion. Some examples of academic dishonesty are cheating, plagiarism, Internet plagiarism, obtaining unfair advantage, falsification of records and official documents, and collusion.

Instruction

- ✓ Show all work and calculation
- ✓ Round off all your answer in engineering notation to the hundredth place.
- ✓ All answers should have units, otherwise points will be deducted.
- ✓ Write your answer in the underline and box/circled your answer in your calculations.

Multiple choices: circle only ONE answer

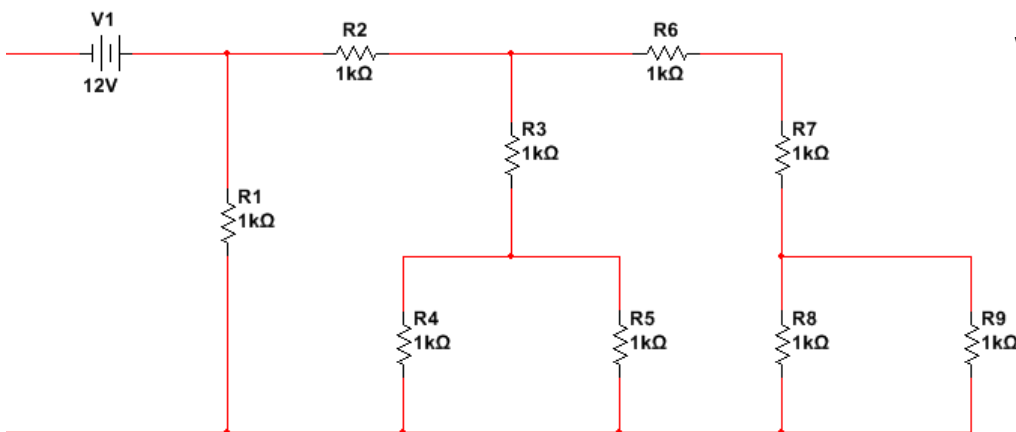For the following network (2 points each):



Which resistor will have 12 V drop?


- a. All of them
- b. R4
- c. R3
- d. R2
- e. R1

Which of the following resistors share **the same current**?

- a. R3 and R4
- b. R1 and R2
- c. R2 and R3
- d. R6 and R7
- e. R7 and R8

Which of the following resistors share **the same voltage**?


- a. R1 and R3
 - b. R1 and R4
 - c. R3 and R7
 - d. R5 and R8
 - e. R8 and R9
-

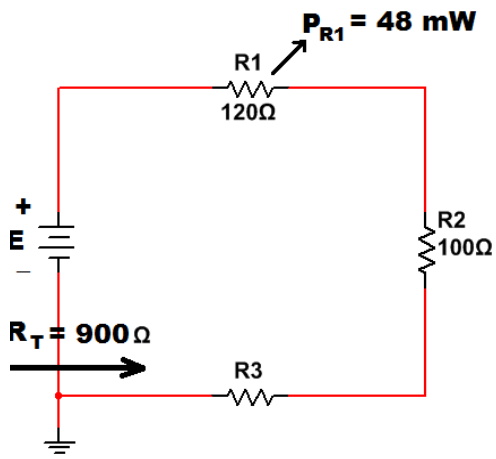

Question 1

For the following circuit, solve for:


- Resistance in R_3 (3 points) _____
- Voltage source, E (4 points) _____

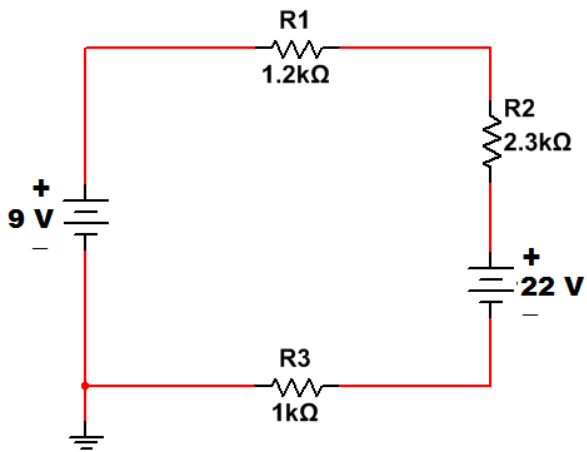

Question 2

For the following circuit, solve for:


- Current source, I_s (4 points) _____
- Voltage drop in R_1 , V_{R1} (3 points) _____
- Voltage drop in R_2 , V_{R2} (3 points) _____
- Voltage drop in R_3 , V_{R3} (3 points) _____
- Show the direction of the current within the closed path and the polarity of each voltage drop for each resistor in the series circuit (2.5 points)

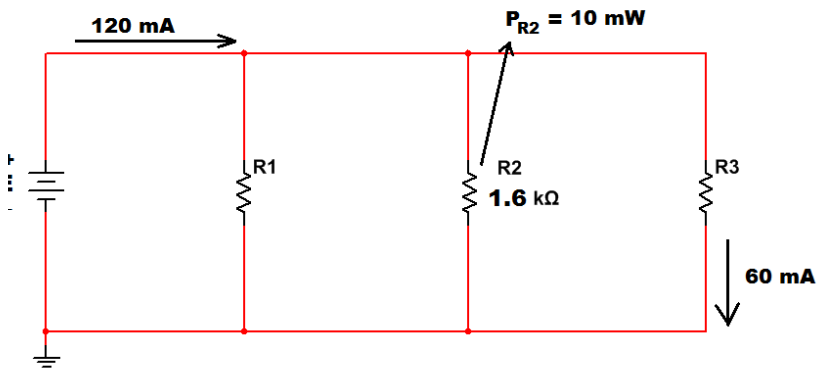

Question 3

For the following circuit:

- Voltage source, E (4 points) _____
- Total resistance, R_T (3 points) _____
- Resistance in R_3 (3 points) _____
- Resistance in R_1 (3 points) _____

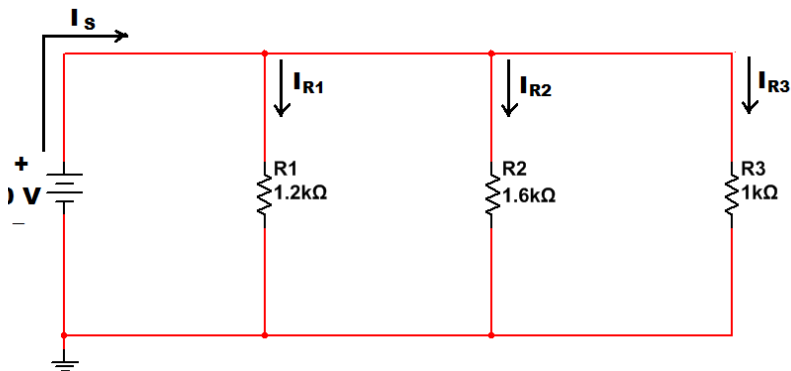


Question 4

For the following circuit, find:

- Total resistance, R_T (4 points) _____
- Current source, I_s (3 points) _____
- Current through R_3 (3 points) _____

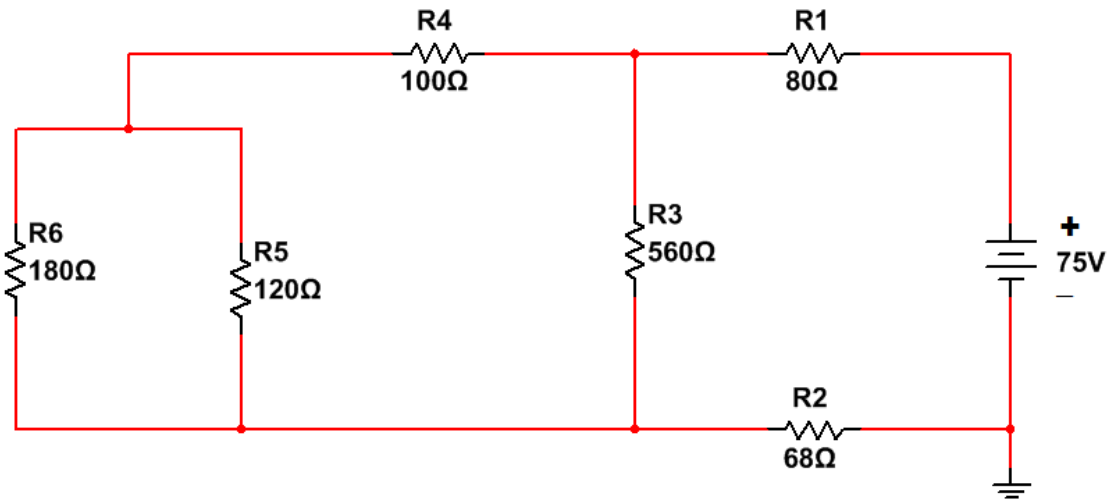Question 5

For the following series-parallel circuit, find



- Total resistance, R_T (6 points) _____
- Voltage in R_1 , V_{R1} (2 points) _____
- Voltage in R_2 , V_{R2} (2 points) _____
- Voltage in R_3 , V_{R3} (2 points) _____
- Voltage in R_4 , V_{R4} (3 points) _____
- Voltage in R_5 , V_{R5} (3 points) _____
- Voltage in R_6 , V_{R6} (2 points) _____
- Current through R_1 , I_{R1} (2 points) _____
- Current through R_2 , I_{R2} (2 points) _____
- Current through R_3 , I_{R3} (2 points) _____
- Current through R_4 , I_{R4} (3 points) _____
- Current through R_5 , I_{R5} (3 points) _____
- Current through R_6 , I_{R6} (3 points) _____